

# CO502-2021 : Advanced Computer Architecture

## Part 4 (Hazard Control)

### Group 4

#### Data Path

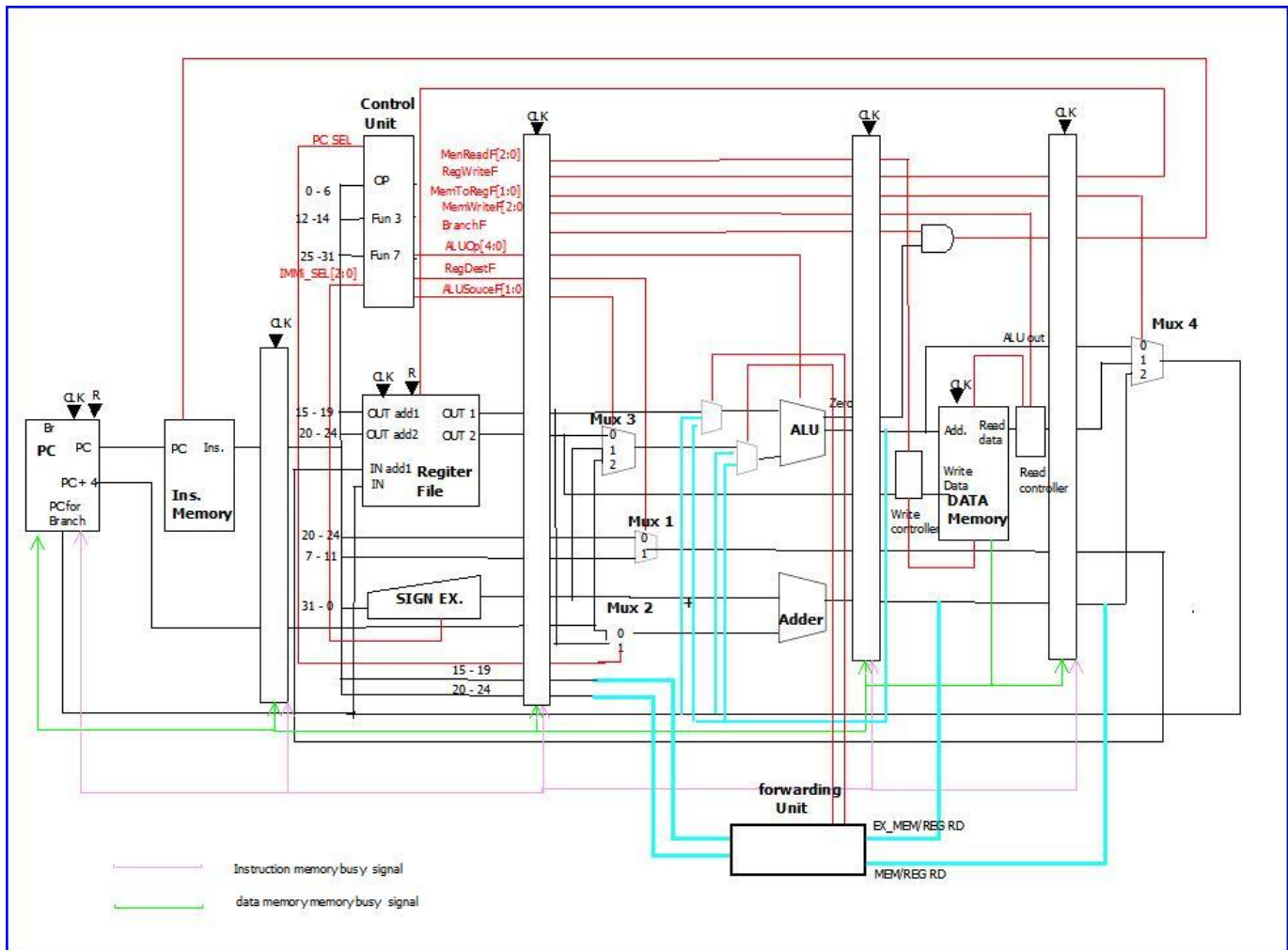


FIGURE 1 - Data path

# Hardware Units

## 1. ALU - Arithmetic Logic Unit

 


FIGURE 2 - ALU design

Inputs :

`DATA1[31:0]` - 32 bit operand 1

`DATA2[31:0]` - 32 bit operand 2

`SELECT[4:0]` - 5 bit ALUOp

Output :

`RESULT[31:0]` - 32 bit ALU Result

`BRANCH` - 1 bit Branch Result (which used for branch instructions)

- In the alu the main function is getting 2 DATA inputs and do the operation according to the SELECT(which contain the alu opcodes) and give RESULT and BRANCH as output.
- 5 bits are assigned for ALUOp and 32 options for SELECT. And used 17 options for giving various RESULT outputs. And used another 6 for giving BRANCH output. If there is no RESULT or BRANCH output needed for an ALUOp it returns 0 as default.

The ALUOps assigned as Table 1 for operation,

ALUOP[4:0]	RESULT[31:0]	BRANCH
00000	RES_ADD	0
00001	RES_SLL	0
00010	RES_SLT	0
00011	RES_SLTU	0
00100	RES_XOR	0
00101	RES_SRL	0
00110	RES_OR	0
00111	RES_AND	0
01000	0	BR_BEQ
01001	0	BR_BNE
01010	0	0
01011	0	0
01100	0	RES_BLT
01101	0	RES_BGE
01110	0	RES_BLTU
01111	0	RES_BGEU
10000	RES_SUB	0
10001	RES_FWD	1
10010	0	0
10011	0	0
10100	0	0
10101	0	0
10110	0	0
10111	0	0
11000	RES_MUL	0
11001	RES_MULH	0
11010	RES_MULHSU	0
11011	RES_MULHU	0
11100	RES_DIV	0
11101	RES_REM	0
11110	RES_FWD	0
11111	RES_REMU	0

Table 1 : ALU Op codes

- ALL the operation takes DATA2 which comes through the multiplexer therefore as an initial plan set 2 time unit delay.
- RESULT gives in 32 bit binary format therefore values which contain more than 32 bit send RESULT by negotiating extra bits. Therefore, It can't do a calculation where the result value exceeds the 32 bit and can't give the exact correct answers.
- The ALU module is tested using a test bench and all the functions work properly in the ALU model test.

## 2. Register File

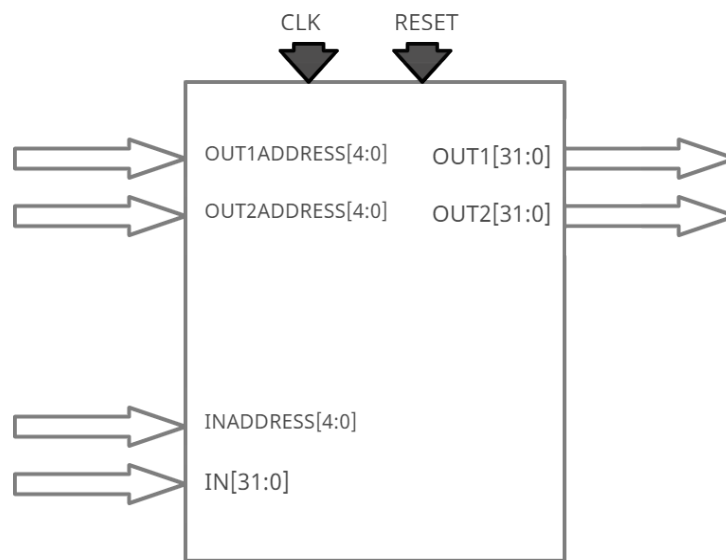


FIGURE 3 : Register file design

### Inputs:

- OUT1ADDRESS [4:0] - address of OUT1 (data which is read from the register file)
- OUT2ADDRESS [4:0] - address of OUT2 (data which read from the register file)
- INADDRESS[4:0] - address of IN (Data which is written on the register file)
- IN [31:0] - The which need to write a register file
- WRITEANABLE - the signal to enable the writing data on the register. This is 1 when I need to write on register
- CLK - clock
- RESET- result signal

### Outputs:

OUT1 [31:0] -	Data value 1 read from the register according to the
OUT1ADDRESS	
OUT1 [31:0] -	Data value 1 read from the register according to the
OUT1ADDRESS	

The register file can keep 32 data values of 32 bits (4 Bytes).  
 After 2 time units Writing will happen to the Register.

### 3. Control Unit

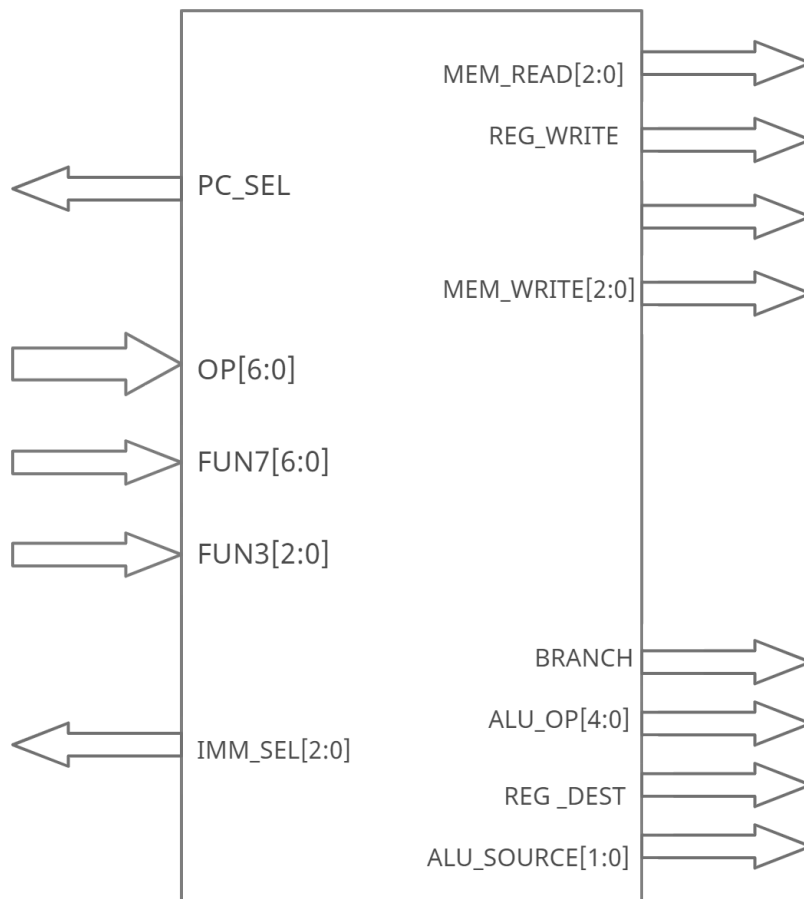


FIGURE 4 : Control unit design

Inputs :

OPCODE[6:0]            - opcode of the instruction  
 FUN7[6:0]             - function 7 of the instruction  
 FUN3[2:0]             -function 3 of the instruction

Outputs :

Memory Read Flag  
 Register write Flag  
 Memory Write flag  
 Memory to register flag  
 Branch flag  
 Alu opcode  
 Register destination flag  
 Alu source flag  
 Immediate value selector  
 PC selector

There are 10 control signals which are controlled by this unit.

Instruction	Type	MEM read	MEM Write	Memory to reg	REG write	ALU source	Branch	Register destination	IMM_SEL	PC_SEL
LB	I-Type	1	0	1	1	1	0	1	0	x
LH	I-Type	2	0	1	1	1	0	1	0	x
LW	I-Type	3	0	1	1	1	0	1	0	x
LBU	I-Type	4	0	1	1	1	0	1	0	x
LHU	I-Type	5	0	1	1	1	0	1	0	x
ADDI	I-Type	0	0	0	1	1	0	1	0	x
SLTI	I-Type	0	0	0	1	1	0	1	0	x
SLTIU	I-Type	0	0	0	1	1	0	1	0	x
XORI	I-Type	0	0	0	1	1	0	1	0	x
ORI	I-Type	0	0	0	1	1	0	1	0	x
ANDI	I-Type	0	0	0	1	1	0	1	0	x
SLLI	I-Type	0	0	0	1	1	0	1	1	x
SRLI	I-Type	0	0	0	1	1	0	1	1	x
SRAI	I-Type	0	0	0	1	1	0	1	1	x
SB	S-Type	0	1	x	0	1	0	x	2	x

SH	S-Type	0	2	x	0	1	0	x	2	x
SW	S-Type	0	3	x	0	1	0	x	2	x
SBU	S-Type	0	4	x	0	1	0	x	2	x
SHU	S-Type	0	5	x	0	1	0	x	2	x
ADD	R-Type	0	0	0	1	0	0	1	x	x
SUB	R-Type	0	0	0	1	0	0	1	x	x
SLL	R-Type	0	0	0	1	0	0	1	x	x
SLT	R-Type	0	0	0	1	0	0	1	x	x
SLTU	R-Type	0	0	0	1	0	0	1	x	x
XOR	R-Type	0	0	0	1	0	0	1	x	x
SRL	R-Type	0	0	0	1	0	0	1	x	x
SRA	R-Type	0	0	0	1	0	0	1	x	x
OR	R-Type	0	0	0	1	0	0	1	x	x
AND	R-Type	0	0	0	1	0	0	1	x	x
MUL	R-Type	0	0	0	1	0	0	1	x	x
MULH	R-Type	0	0	0	1	0	0	1	x	x
MULHS U	R-Type	0	0	0	1	0	0	1	x	x
MULHU	R-Type	0	0	0	1	0	0	1	x	x
DIV	R-Type	0	0	0	1	0	0	1	x	x
REM	R-Type	0	0	0	1	0	0	1	x	x
REMU	R-Type	0	0	0	1	0	0	1	x	x
LUI	U-type	0	0	0	1	1	0	1	3	x
AUIPC	U-type	0	0	2	1	x	0	1	3	x
JALR	I-Type	0	0	0	1	2	1	1	3	0
JAL	J-Type	0	0	0	1	2	1	1	3	1
BEQ	B-Type	0	0	2	0	0	1	x	2	0
BNE	B-Type	0	0	2	0	0	1	x	2	0
BLT	B-Type	0	0	2	0	0	1	x	2	0
BGE	B-Type	0	0	2	0	0	1	x	2	0
BLTU	B-Type	0	0	2	0	0	1	x	2	0
BGEU	B-Type	0	0	2	0	0	1	x	2	0

Table 2 : Instruction with control signals

Follow [this link](#) for control signals with all ALU op codes.(Sheet 3)

- To process S type and J type instructions 2 new control signals are added(immediate value selector and PC selector).Since there are few types of immediate value range selections,a new Immediate value selector control signal is there and which will be processed in the Sign extender unit.
- Also there connection is made between ALU and the PC value,because of JAL and JALR instructions.Because they write PC value to the source register.
- Also there is another wire to connect the PC adder and ALU output to process branch instructions and U-type instructions.
- There are no time delays for the control unit signal generation.
- And also signals are generated asynchronously.

#### 4. Programme Counter

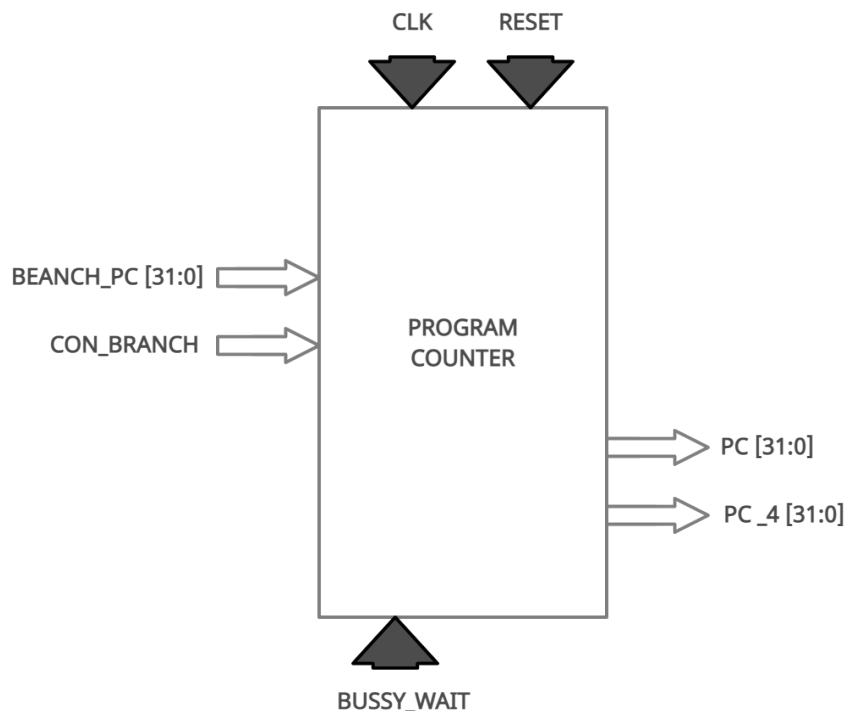




FIGURE 5 : PC unit design

Inputs:

BRANCH\_PC - control signal for branch instructions  
Branch\_pc - Programme counter value when a branch is happening  
CLK - clock  
RESET- result signal

Outputs:

PC - Programme counter value  
PC - programme counter value + 4

- signals are generated synchronously.
- If the BUSY WAIT and BRANCH control signals are zero, the positive edge at the clock signal PC value will be updated (increased by 4) .
- If the BRANCH control signal is 1, branch will happen according to the BRANCH PC value.
- The PC\_4 output value is used to predict the new PC value for branch instructions and u-type instructions.

## Instruction memory hierarchy

- Instruction cache module is directly connected to the CPU while instruction memory is connected to the cache.
- Cache module has 8 data arrays with 4 instructions wide.
- When there is a miss instruction cache, communicate with the instruction memory and read 4 instructions wide data. It will take about 10 clock cycles and in the meantime processor is stalled using the busy wait signals. Intermediate Busy signal is used to communicate with cache and the memory.

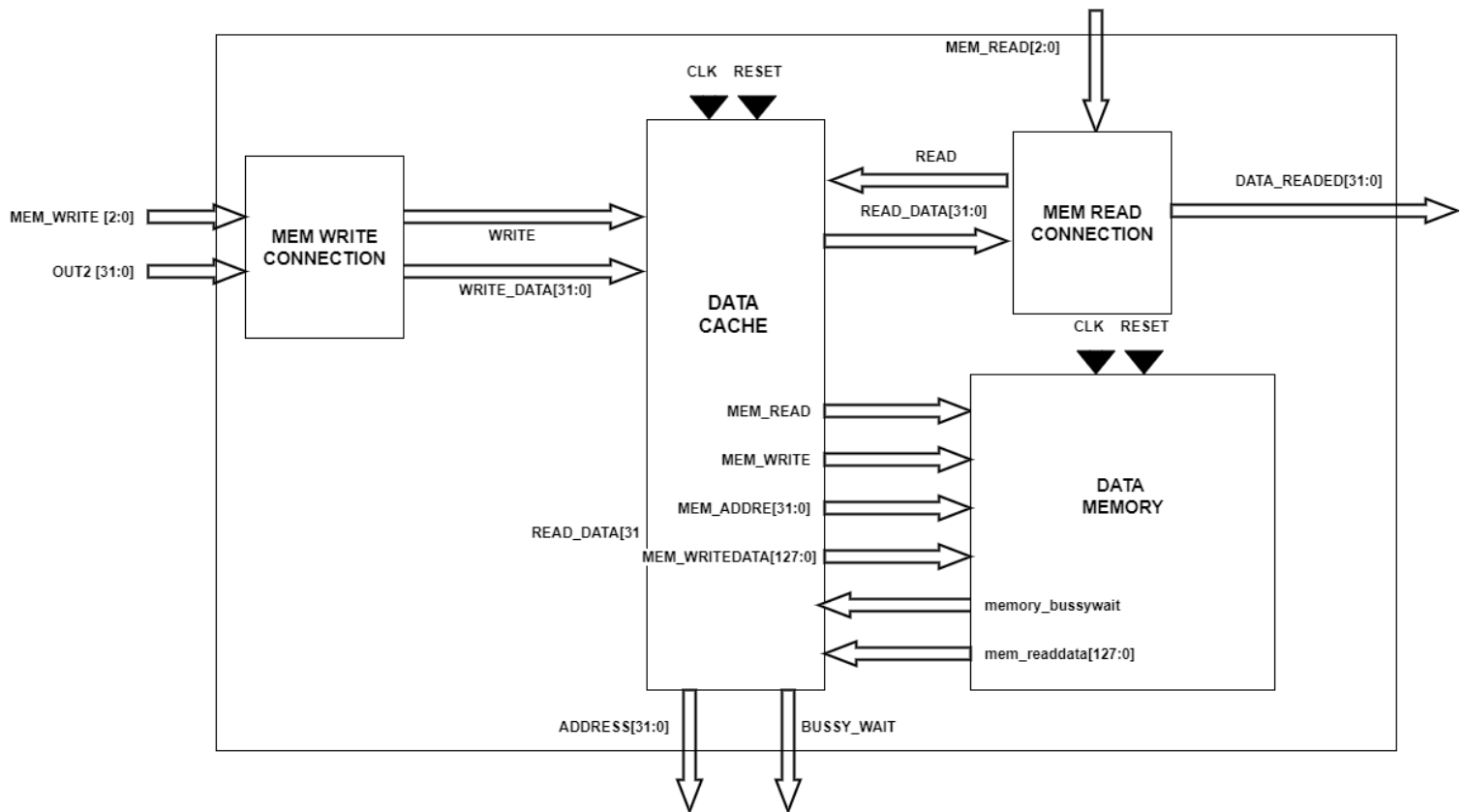


FIGURE 6 : Data Memory hierarchy

## Data memory hierarchy

- Data cache module is directly connected to the cpu while Data memory is connected to the cache.
- Cache module has 8 data arrays 4 words wide.
- Write back policy is used in data memory hierarchy.
- Same as the instruction memory ,It will take about 10 clock cycles when there is a miss and in the meantime processor is stolen using the busy wait signals.Intermediate Busy signal is used to communicate with cache and the memory.

## Read And Write Controller

- As figure 2 shows there are Two modules between the data cache and other modules.
- Those modules are there to handle special Memory read and write Instruction like LH,LB,SB,SH.

- According to the Opcode ,3 bit long control signals are sent to those modules and These modules will filter Byte or a half word from the data reading or Writing.
- And also those modules generate the write or read control signal for the data cache according to the 3 bit control signal coming from the control unit.

## **Pipeline Registers**

There are four pipeline registers to connect the 5 stages of the RISC-V processor. The for pipeline registers are,

- Pipeline 1 (IF-ID Pipeline)
- Pipeline 2 (ID-EX Pipeline)
- Pipeline 3 (EX-MEM pipeline)
- Pipeline 4 (MEM-WB pipeline)

All the pipeline sends data to next stages with time units delay according to the need.

## 1. Pipeline1 (IF\_ID\_Pipeline) Register

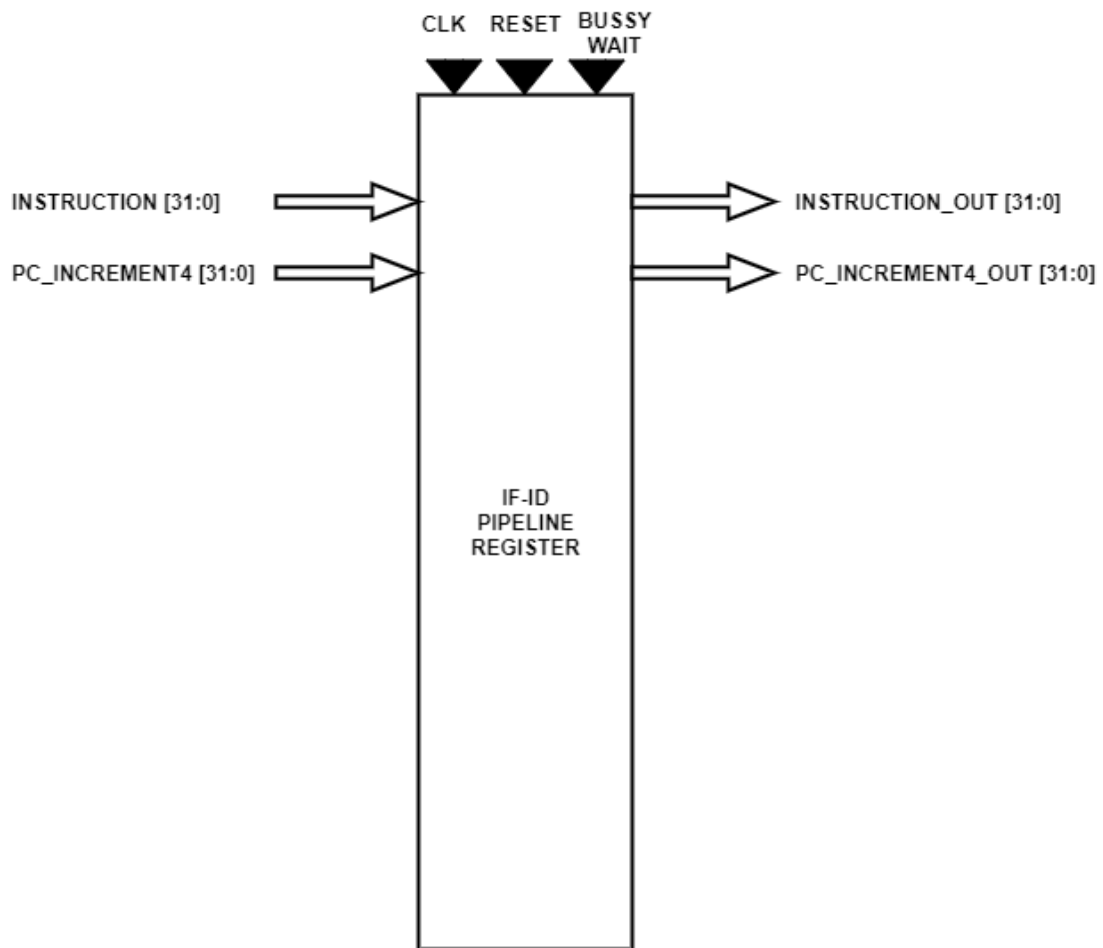


FIGURE 7: IF-ID Pipeline Register

Inputs: CLK

RESET

BUSSY\_WAIT

INSTRUCTION [31:0]

PC\_INCREMENT4 [31:0]

Outputs:

INSTRUCTION\_OUT [31:0]

PC\_INCREMENT4\_OUT [31:0]

Time Delays:

After positive clock edge 1 time unit delay added to set INSTRUCTION\_OUT

- This pipeline register is located in between Instruction Fetching and Instruction decoding stages.

- The BUSSY\_WAIT signal is to decide whether the data need to be set for the next stage or wait. Because when Instruction memory or Data memory busy need to hold the data on the pipeline to freeze the system.
- When the RESET signal is 1 set INSTRUCTION\_OUT to 0 and PC\_INCREMENT4\_OUT to -4 to reset the processor.

## 2. Pipeline2 (ID\_EX\_Pipeline) Register

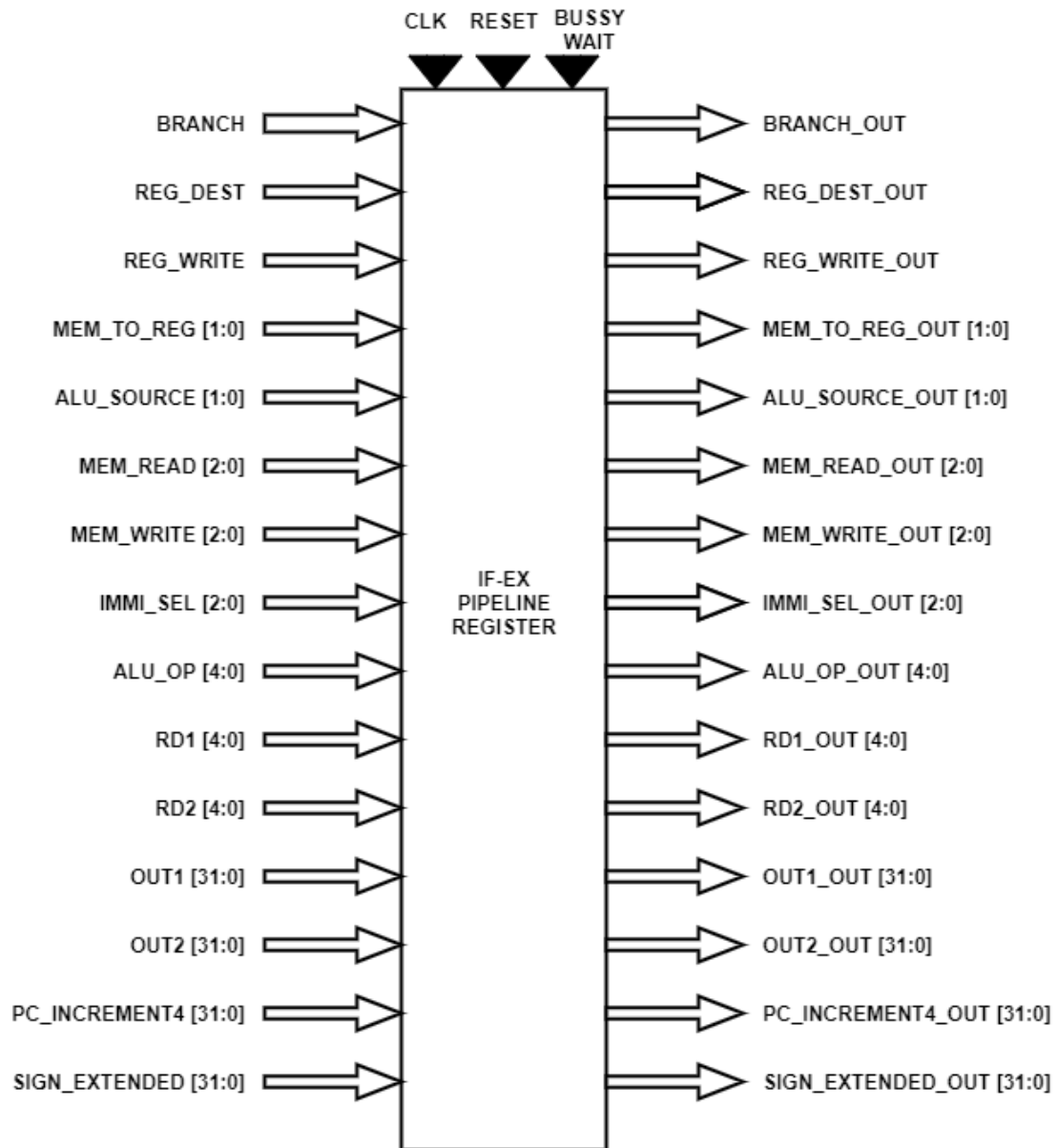


FIGURE 8: ID-EX Pipeline Register

Inputs: CLK  
 RESET  
 BUSSY\_WAIT  
 BRANCH

REG\_DEST  
REG\_WRITE  
PC\_SEL  
MEM\_TO\_REG [1:0]  
ALU\_SOURCE [1:0]  
MEM\_READ [2:0]  
MEM\_WRITE [2:0]  
IMMI\_SEL [2:0]  
ALU\_OP [4:0]  
RD1 [4:0] - Register Destination 1  
RD2 [4:0] - Register Destination 2  
OUT1 [31:0] - Data 1 from register file  
OUT2 [31:0] - Data 2 from register file  
PC\_INCREMENT4 [31:0]  
SIGN\_EXTENDED [31:0]

#### Outputs:

BRANCH\_OUT  
REG\_DEST\_OUT  
REG\_WRITE\_OUT  
PC\_SEL\_OUT  
MEM\_TO\_REG\_OUT [1:0]  
ALU\_SOURCE\_OUT [1:0]  
MEM\_READ\_OUT [2:0]  
MEM\_WRITE\_OUT [2:0]  
IMMI\_SEL\_OUT [2:0]  
ALU\_OP\_OUT [4:0]  
RD1\_OUT [4:0] - Register Destination 1  
RD2\_OUT [4:0] - Register Destination 2  
OUT1\_OUT [31:0] - Data 1 from register file  
OUT2\_OUT [31:0] - Data 2 from register file  
PC\_INCREMENT4\_OUT [31:0]  
SIGN\_EXTENDED\_OUT [31:0]

#### Time Delay:

Add 3 time units delays after the positive clock edge for setting input values to **MEM\_TO\_REG & REG\_WRITE** output registers output registers. Because that data flows directly through the next two pipelines (EX-MEM pipeline & MEM-WB pipeline). To prevent overwriting data in two pipelines before sending data to the next stage added this delay.

Add 2 time units delays after the positive clock edge for setting input values to **BRANCH\_OUT**, **MEM\_READ\_OUT** & **MEM\_WRITE** output registers. Because that data goes directly to the next pipeline(EX-MEM Pipeline) without going through any modules. Therefore add additional time unit delay to prevent overwriting data before sending to the next stage in the EX-MEM pipeline.

Add 1 time unit delays for setting all other output registers values.

- This pipeline register is located in between the Instruction decoding process and ALU.
- The BUSSY\_WAIT signal is to decide whether the data need to be set for the next stage or wait. Because when Instruction memory or Data memory busy need to hold the data on the pipeline to freeze the system.
- When the RESET signal is 1 set PC\_INCREMENT4\_OUT to -4 and all other output register values to 0 to reset the processor.

### 3. Pipeline3 (EX\_MEM\_Pipeline) Register

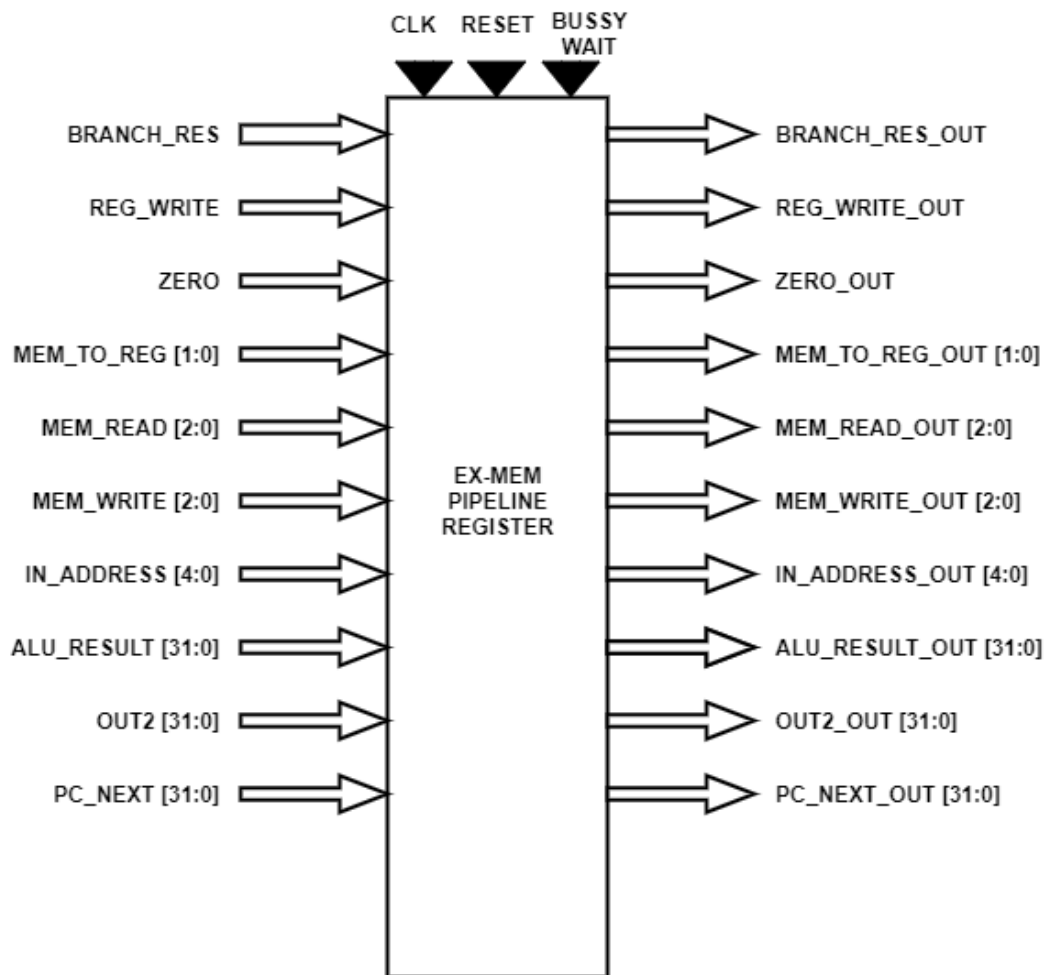


FIGURE 9: EX-MEM Pipeline Register

Inputs: CLK

RESET

BUSSY\_WAIT

BRANCH\_RES - Alu result for the branch

REG\_DEST

REG\_WRITE

MEM\_TO\_REG [1:0]

MEM\_READ [2:0]

MEM\_WRITE [2:0]

IN\_ADDRESS [4:0] - address where the data need to write on register file

ALU\_RESULT [31:0]

OUT2 [31:0] -

PC\_NEXT [31:0]

Outputs:

BRANCH\_RES\_OUT - Alu result for the branch



REG\_DEST\_OUT

REG\_WRITE\_OUT

MEM\_TO\_REG\_OUT [1:0]

MEM\_READ\_OUT [2:0]

MEM\_WRITE\_OUT [2:0]

IN\_ADDRESS\_OUT [4:0] - address where the data need to write on register file

ALU\_RESULT\_OUT [31:0]

OUT2\_OUT [31:0]

Time Delays:

Add 2 time units delays after the positive clock edge for setting input values to **REG\_WRITE\_OUT, MEM\_TO\_REG\_OUT, PC\_NEXT\_OUT & IN\_ADDRESS\_OUT** output registers. Because that data goes directly to the next pipeline(MEM\_WB Pipeline) without going through any modules. Therefore add additional time unit delay to prevent overwriting data before sending to the next stage in the MEM-WB pipeline.

Add 1 time unit delays for setting all other output registers values.

- This pipeline register is located in between the ALU and Memory.
- The BUSSY\_WAIT signal is to decide whether the data need to be set for the next stage or wait. Because when Instruction memory or Data memory busy need to hold the data on the pipeline to freeze the system.
- When the RESET signal is 1 set all the output register values to 0 to reset the processor.

#### 4. Pipeline4 (MEM-WB\_Pipeline) Register

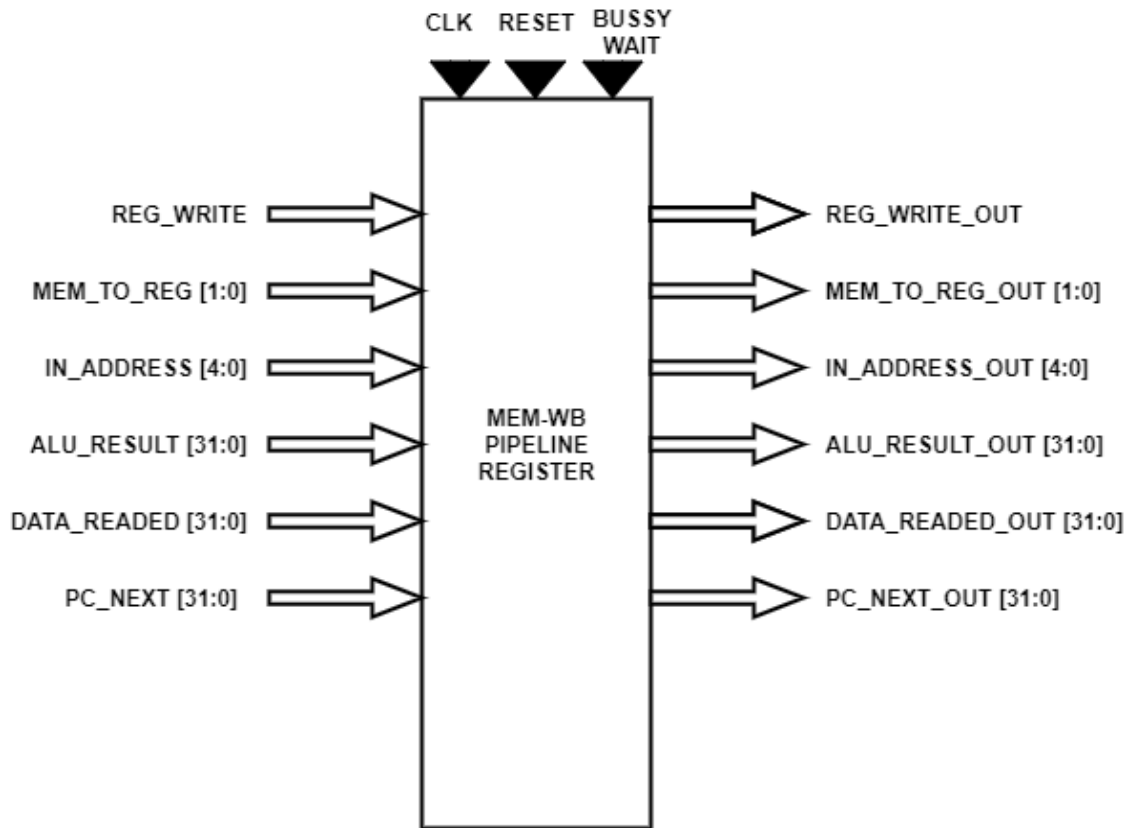


FIGURE 10: EX-MEM Pipeline Register

Inputs: CLK

RESET

BUSSY\_WAIT

REG\_WRITE

MEM\_TO\_REG [1:0]

IN\_ADDRESS [4:0] - address where the data need to write on register file

ALU\_RESULT [31:0]

DATA\_READED [31:0]

PC\_NEXT [31:0]

Outputs:

REG\_WRITE\_OUT

MEM\_TO\_REG\_OUT [1:0]

IN\_ADDRESS\_OUT [4:0] - address where the data need to write on register file

ALU\_RESULT\_OUT [31:0]

PC\_NEXT\_OUT [31:0]

DATA\_READED [31:0]

Time Delays:

Add 1 time unit delay for setting all output registers values.

- This pipeline register is located in between the MEMORY stage and WRITEBACK stages.
- The BUSSY\_WAIT signal is to decide whether the data need to be set for the next stage or wait. Because when Instruction memory or Data memory busy need to hold the data on the pipeline to freeze the system.
- When the RESET signal is 1 set all the output register values to 0 to reset the processor.

## Forwarding Unit

The forwarding unit was implemented to control the data hazard which occurred when reading register values. To control this forward values from MEMORY and WRITEBACK stages if there is any data hazard

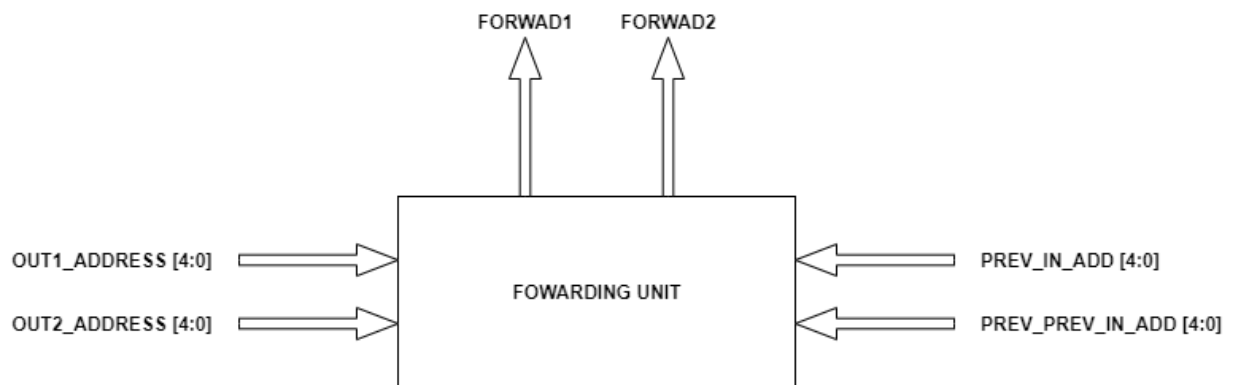


FIGURE 11 - Diagram of Forwarding Unit

INPUTS: OUT1\_ADDRESS [4:0]- Read register address 1 of current instruction on EX stage  
OUT2\_ADDRESS [4:0]- Read register address 2 of current instruction on EX stage  
PREV\_IN\_ADD[4:0] - Write register address of instruction in Memory stage  
PREV\_PREV\_IN\_ADD[4:0]-Write register address of instruction in WB stage

OUTPUTS: FORWAD1[1:0] - Select signal for ALU mux1  
FORWAD2[1:0] - Select signal for ALU mux2

In this unit compare the OUT1\_ADDRESS & OUT2\_ADDRESS with PREV\_IN\_ADD & PREV\_PREV\_IN\_ADD separately and generate the FORWARD signals. Thos signal generation done according to this condition below,

Condition	FORWAD1
OUT1_ADDRESS not equal both	0
OUT1_ADDRESS equal to PREV_IN_ADD	1
OU1_ADDRESS not equal PREV_IN_ADD and equal to PRE_PREV_IN_ADD	2

Condition	FORWAD2
OUT2_ADDRESS not equal both	0
OUT2_ADDRESS equal to PREV_IN_ADD	1
OU2_ADDRESS not equal PREV_IN_ADD and equal to PRE_PREV_IN_ADD	2

This is how the forwarding unit handles data hazard by bypassing the values.

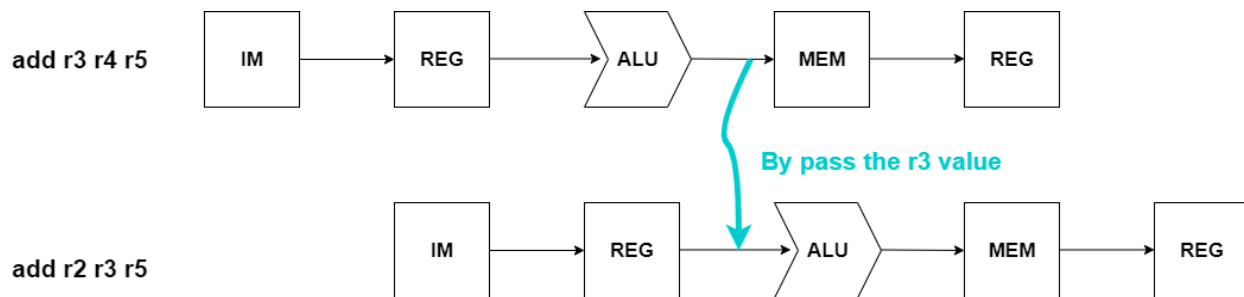


FIGURE 12 : Bypassing data from previous instruction

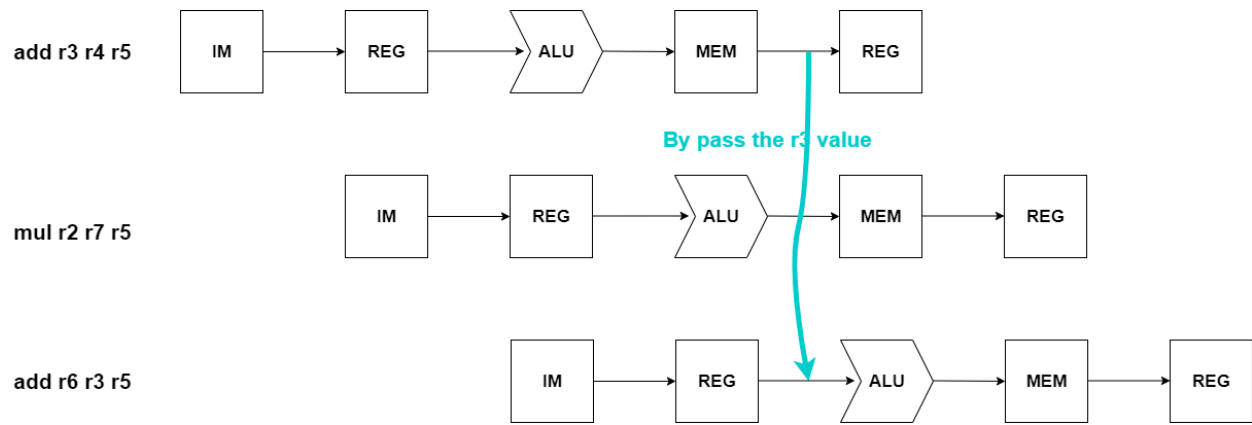


FIGURE 13 : Bypassing data from previous instruction

## ALU Mux1

This module is implemented to choose the relevant DATA1 according to the FOWARD1 value.

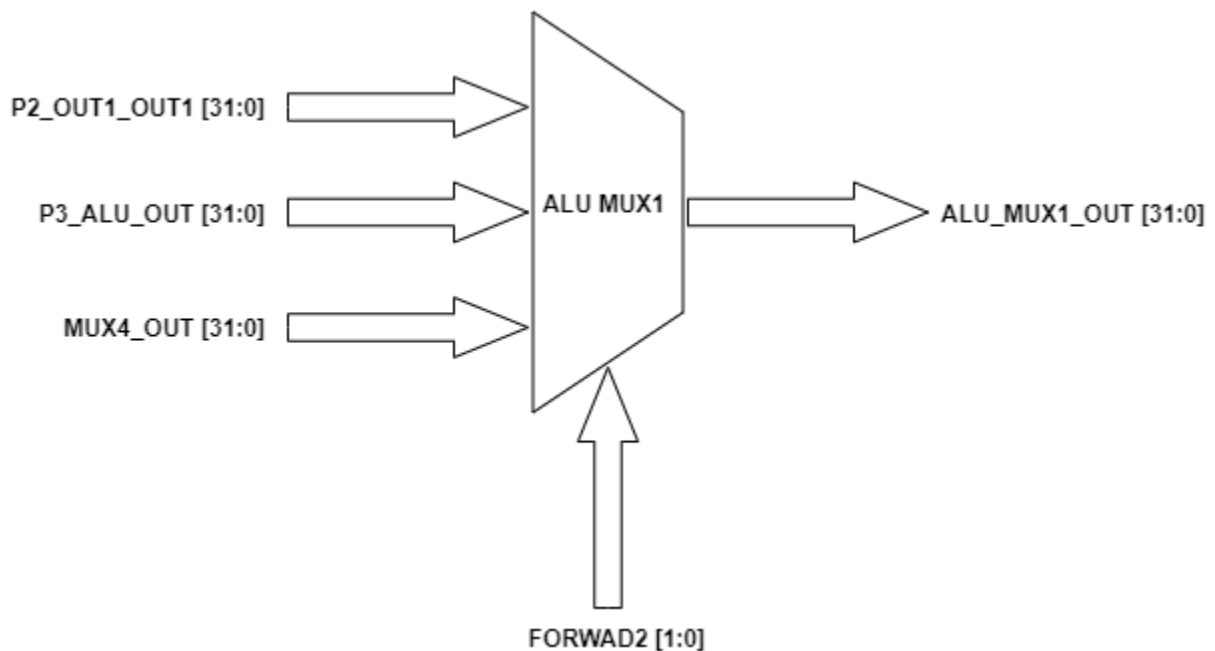


FIGURE 14 : ALU MUX1 Diagram

### INPUTS :

P2\_OUT1\_OUT - Data read from the register

P3\_ALU\_OUT - ALU result value from the previous instruction

MUX4\_OUT - Register Write data from 2nd Previous instruction.

FORWAD1

### OUTPUT:

ALU\_MUX1\_OUT - Data value 1 to the ALU

Addea one time unite delay in the mosule

## ALU Mux2

This module is implemented to choose the relevant DATA2 according to the FOWARD1 value.

 


FIGURE 15 : ALU MUX1 Diagram

### INPUTS :

- MUX3\_OUT - Data 2 value from register or immediate value
- P3\_ALU\_OUT - ALU result value from the previous instruction
- MUX4\_OUT - Register Write data from 2nd Previous instruction.
- FORWAD1

### OUTPUT:

- ALU\_MUX2\_OUT - Data value 2 to the ALU

Addea one time unite delay in the mosule

## Timing

Stage	Process	Timing
Stage1: Instruction Fetch	1.PC update	3

	2.Instruction tag comparison	1
	3.Output the the instructions	1
Stage 2: Instruction Decode	1.Output pipeline data	1
	2.Generating control signals	1
	3.Data writes to register	3
	4.Data Reads from register	5
	5.Sign extender	1
Stage3 : Instruction Execut	1.Output pipeline data	1
	2.Mux 3	1
	3.Mux 2	1
	4.Mux 1	1
	5.ALU Mux1	1
	6.ALU Mux1	1
	7.ALU	2
	8.Adder	2
Stage 4:Memory Access	1.Output pipeline data	1
	2.And gate	1
	3.Write controller	1
	4.read Controller	1
	5.Data Memory Write	2
	6.Data Memory Read	5
Stage5: Write Back	1.Output pipeline data	1
	2.Mux 4	1

	3. Write back	3
--	---------------	---

Table 3: Timing delays

 




FIGURE 16: Timing diagram

- Pipeline data forwarding, register file writing and PC updating happen synchronously to the clock while Other modules do not.
- PC updating happens after 3ns delay after receiving the Branch signal which takes 2ns.
- Since the register write back happen in synchronously, for data writing back there is 3ns delay. Because of writing data will be available at the register file only after 2ns (pipeline delay + MUX 4 delay)
- Pipeline data forwarding happen at the rising clock edge after 1ns of delay. But except for the pipeline signals which are not used in the current stage. As a example in 3rd stage (Instruction Execute stage) AluOp code, RegDef and AluSource signals are forwarding after 1ns and Other siglas like BranchF takes 2ns to forward. Those 2ns delays are there Because of the Other wise Those type of signals can be forwarded to next stage also at the same clock cycle.
- When register reading ,it waits 5 ns from address reserving because the reading should be done after the register writing completes.
- Same as the register file reading also in the memory reading waits 5ns, because it gives time to update the memory.

## **Changes made to other Unit after phase 3**

### **1. Pipeline Register 2**

Pipeline Register 2 change by passing OUT1\_ADDRESS & OUT2\_ADDRESS to the pipeline register. Because I need those two in the forwarding unit.

### **2. Assembler**

Remove the stall made to handle the data hazard because data hazard handling in the forwarding unit.

### **3. ALU**

Additional 1 time unit delay was added for all instructions because ALU Mux modules were added before the ALU and those ALU Mux modules had 1 time unit delay.

### **4. Delay**

New module Delay implemented to give addition 1 time unit delay when Prev\_IN\_ADD pass through the pipeline 3 to 4